

**University of Colorado Boulder
ECEE Department**

ECEN 2350 - Digital Logic - Fall 2023

Location: Engineering Center, ECCR 1B40, MWF 1:25PM - 2:15PM

Instructor: Dr. Mona ElHelbawy

Lab #6: FSM Controller

Date of Experiment: November 16th, 2023

Names: Connor Sorrell

Description

In this lab, we will implement several things in order to multiply two 4-bit unsigned binary numbers (our FSM Controller). First, we will put together an accumulator and shift register in order to implement the 4 bit multiplication. Next we will implement a finite state machine. We will then connect the finite state machine to the shift register and accumulator, as well as the universal seven segment code.

Multiply FSM

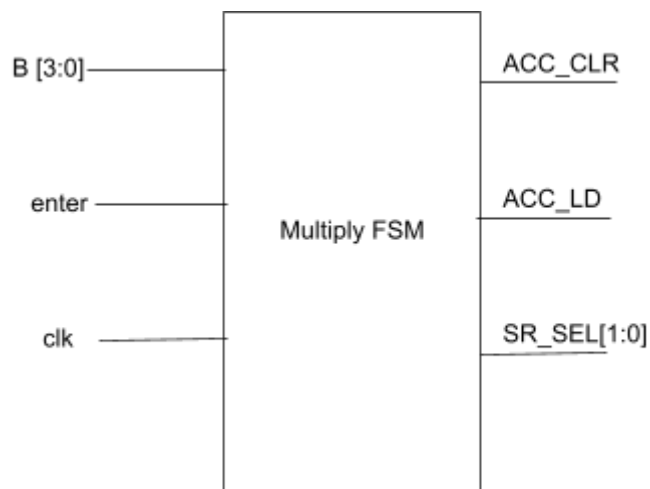


Figure 1.1: Black box diagram of the Multiply FSM showing input and output ports.

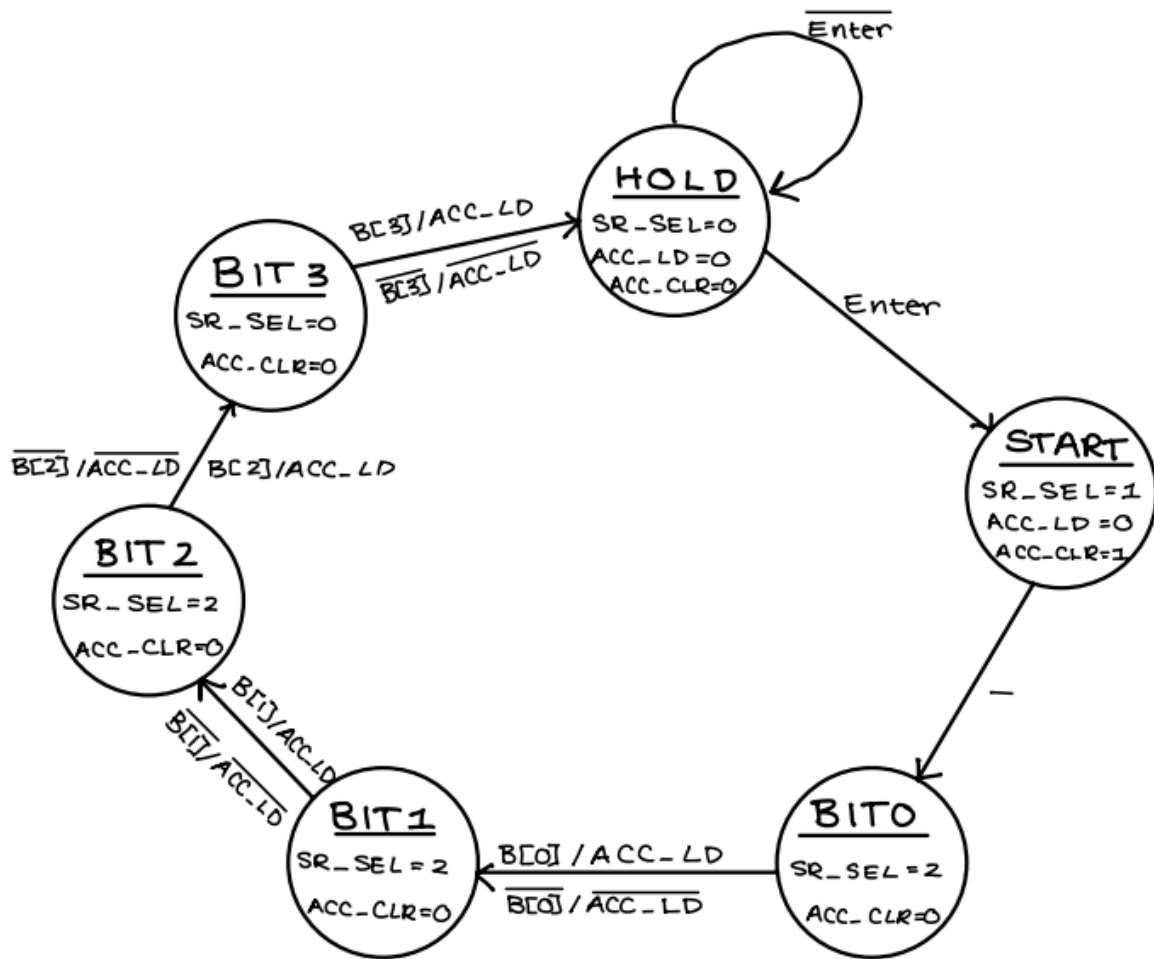


Figure 1.2: FSM State Diagram

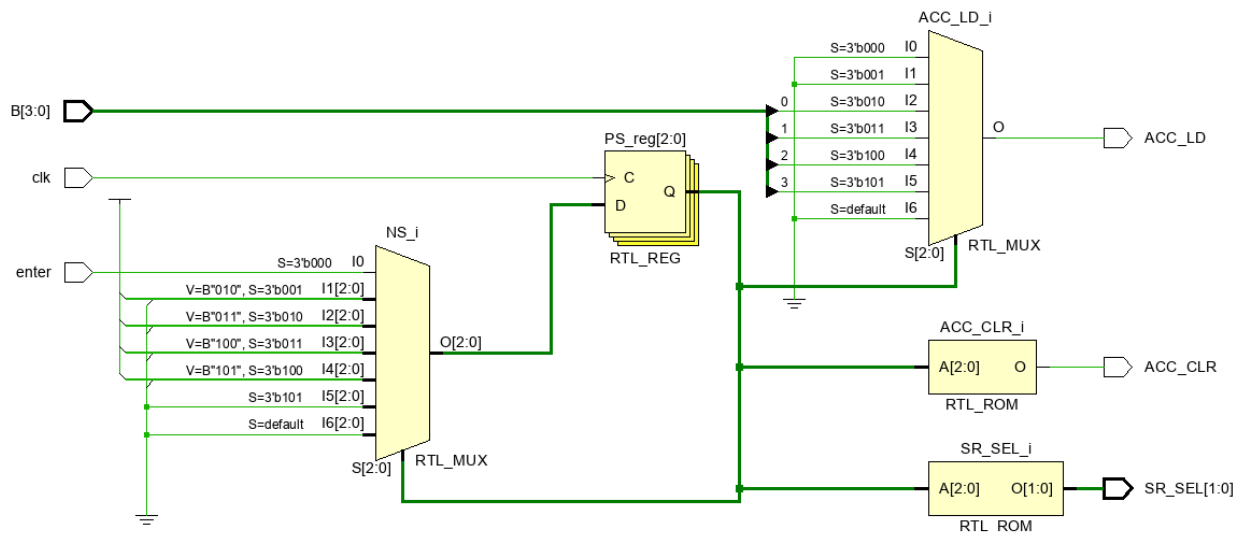


Figure 1.3: Structural Model for the Multiply FSM.

 


Figure 1.4: Simulation timing diagram for the Multiply FSM. Shows the expected intermediate and final outputs.

Multiply FSM Design Code:

```
module FSM(  
    input enter,  
    input clk,  
    input [3:0] B,  
    output logic [1:0] SR_SEL,  
    output logic ACC_LD, ACC_CLR  
);  
  
    logic [2:0] NS;  
    logic [2:0] PS = 0;  
  
    parameter [2:0] HOLD = 3'b000, START = 3'b001, BIT0=3'b010, BIT1 = 3'b011, BIT2 = 3'b100, BIT3 = 3'b101;  
  
    always_ff @ (posedge clk)  
    begin  
        PS <= NS;  
    end  
  
    always_comb  
    begin  
  
        SR_SEL = 0; ACC_LD = 0; ACC_CLR = 0;  
        case(PS)  
            HOLD:begin  
  
                SR_SEL = 0;  
                ACC_LD = 0;  
                ACC_CLR = 0;  
                if (enter)  
                    NS = START;  
                else  
                    NS = HOLD;  
            end  
  
            START:  
            begin  
  
                SR_SEL = 1;  
                ACC_LD = 0;  
                ACC_CLR = 1;  
                NS = BIT0;  
            end  
        end  
    end  
end
```

```

BIT0:
begin
    SR_SEL = 2;
    ACC_CLR = 0;

    if (B[0])
        ACC_LD = 1;
    else
        ACC_LD = 0;
    NS = BIT1;
end

BIT1: begin
    SR_SEL = 2;
    ACC_CLR = 0;
    if(B[1])
        ACC_LD = 1;
    else
        ACC_LD = 0;
    NS=BIT2;
end

BIT2:begin
    SR_SEL = 2;
    ACC_CLR = 0;
    if (B[2])
        ACC_LD = 1;
    NS = BIT3;
end

BIT3:begin
    SR_SEL = 2;
    ACC_CLR = 0;
    if (B[3])
        ACC_LD = 1;
    else
        ACC_LD = 0;
    NS = HOLD;
    end
default:
    NS = HOLD;
endcase
end
endmodule

```

Multiply FSM Sim Code:

```
module FSM_sim();
  logic enter, clk, B, SR_SEL, ACC_LD, ACC_CLR;

  FSM FSM_sim (.*);

  always begin

    clk = 0;
    #1;
    clk = 1;
    #1;

  end

  initial
    begin

      enter = 0;
      B = 4'b0111;
      #20;
      enter = 1;
      #20;
      enter = 0;
      #20;

    end

endmodule
```

Lab 6 Top Module

 


Figure 1.5: Black Box diagram for the Lab 6 Top Module showing the inputs and outputs.

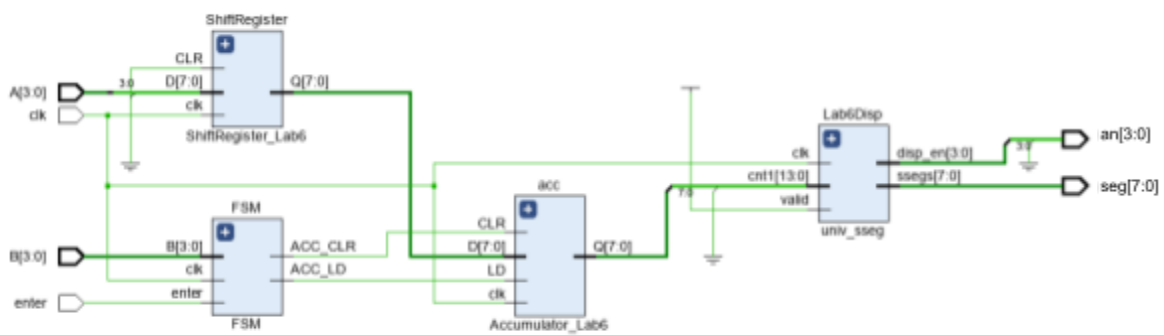


Figure 1.6: Elaborated Design of the Lab 6 Top Level Module

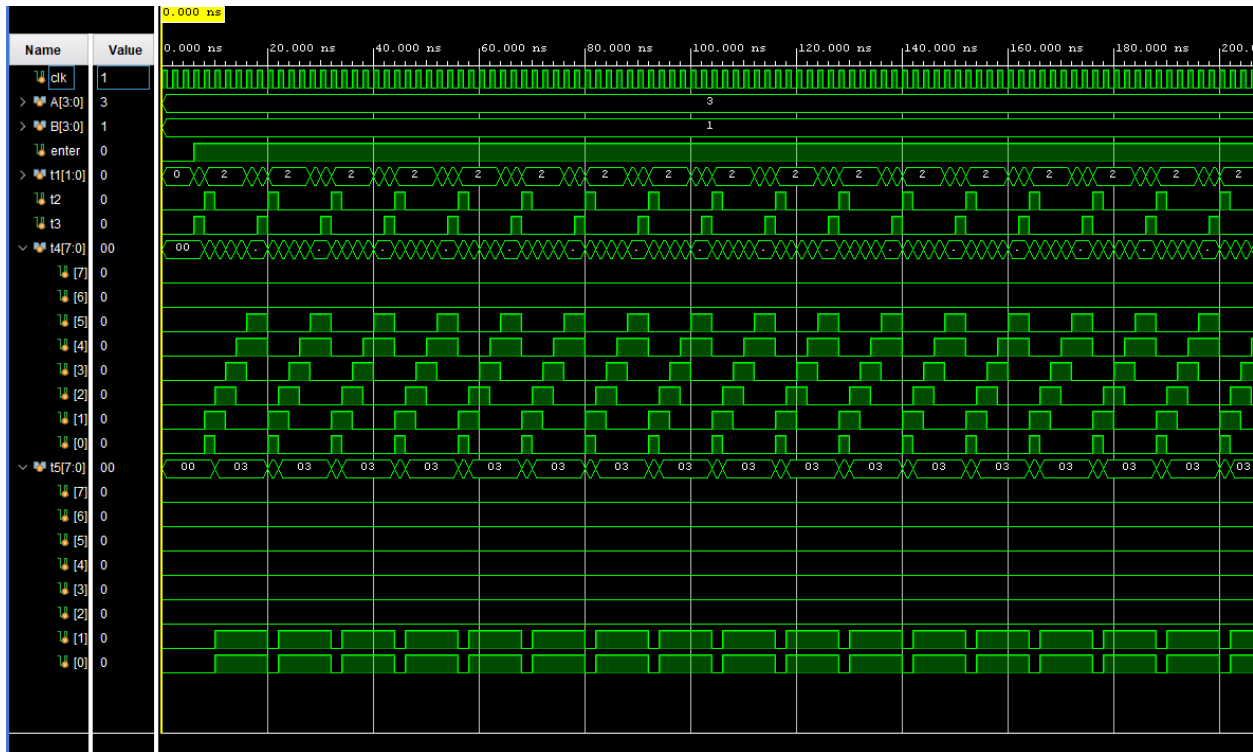


Figure 1.7: Simulation Timing Diagram showing A, B, PS, NS, t1, t2, t3, t4, and t5 intermediate outputs. When enter becomes 1 (4th clock cycle), we start to see values of t2 and t3. They then run through the accumulator and shift register and the intermediate outputs (t5) result as expected.

Lab 6 Top Level Design Code:

```

module Lab6(
    input clk,
    input [3:0] A,
    input [3:0] B,
    input enter,
    output [7:0] seg,
    output [3:0] an
);
    logic [1:0] t1;
    logic t2,t3;
    logic [7:0] t4, t5;

```

```

FSM FSM(.clk(clk), .enter(enter), .B(B), .SR_SEL(t1), .ACC_LD(t2), .ACC_CLR(t3) );
ShiftRegister_Lab6 ShiftRegister (.clk(clk), .CLR(0), .SEL(t2), .D({4'b0,A}), .Q(t4));
Accumulator_Lab6 acc (.clk(clk), .LD(t2), .CLR(t3), .D(t4), .Q(t5));
univ_sseg Lab6Disp (.clk(clk), .cnt1({6'b0,t5}), .valid(1), .ssecs(seg), .disp_en(an));

endmodule

```

Lab 6 Top Level Simulation Code:

```

module Lab6_sim();

```

```

    logic clk;
    logic [3:0] A;
    logic [3:0] B;
    logic enter;
    logic [7:0] seg;
    logic [3:0] an;

```

```

    Lab6 sim(. *);

```

```

    initial begin
        clk = 0;
    end

```

```

    always
    begin
        clk = ~clk;
        #1;
    end

```

```

    initial
    begin
        enter = 0;
        A = 3;
        B = 1;
        #6
        enter = 1;
        #12;
    end
endmodule

```

