

## Lab Report 3

### Connor Sorrell

---

#### Part 1: *Seven Segment Display*

1) BBD

 


Figure 1.1: BBD for the Seven Segment Display

| Decimal | Binary | g<br>seg[6] | f<br>seg[5] | e<br>seg[4] | d<br>seg[3] | c<br>seg[2] | b<br>seg[1] | a<br>seg[0] | Display<br>Value |
|---------|--------|-------------|-------------|-------------|-------------|-------------|-------------|-------------|------------------|
| 0       | 0000   | 1           | 0           | 0           | 0           | 0           | 0           | 0           | 0                |
| 1       | 0001   | 1           | 1           | 1           | 1           | 0           | 0           | 1           | 1                |
| 2       | 0010   | 0           | 1           | 0           | 0           | 1           | 0           | 0           | 2                |
| 3       | 0011   | 0           | 1           | 1           | 0           | 0           | 0           | 0           | 3                |
| 4       | 0100   | 0           | 0           | 1           | 1           | 0           | 0           | 1           | 4                |
| 5       | 0101   | 0           | 0           | 1           | 0           | 0           | 1           | 0           | 5                |
| 6       | 0110   | 0           | 0           | 0           | 0           | 0           | 1           | 0           | 6                |
| 7       | 0111   | 1           | 1           | 1           | 1           | 0           | 0           | 0           | 7                |
| 8       | 1000   | 0           | 0           | 0           | 0           | 0           | 0           | 0           | 8                |
| 9       | 1001   | 0           | 0           | 1           | 1           | 0           | 0           | 0           | 9                |
| 10      | 1010   | 0           | 0           | 0           | 1           | 0           | 0           | 0           | A                |
| 11      | 1011   | 0           | 0           | 0           | 0           | 0           | 1           | 1           | b                |
| 12      | 1100   | 1           | 0           | 0           | 0           | 1           | 1           | 0           | C                |
| 13      | 1101   | 0           | 1           | 0           | 0           | 0           | 0           | 1           | d                |
| 14      | 1110   | 0           | 0           | 0           | 0           | 1           | 1           | 0           | E                |
| 15      | 1111   | 0           | 0           | 0           | 1           | 1           | 1           | 0           | F                |

Figure 1.2: Truth Table for Seven Segment Display

## 2) Circuit Description using *always\_comb* block

```
always_comb
begin
    case(binary)
        4'b0000: seg = 7'b100000;
        4'b0001: seg = 7'b1111001;
        4'b0010: seg = 7'b0100100;
        4'b0011: seg = 7'b0110000;
        4'b0100: seg = 7'b0011001;
        4'b0101: seg = 7'b0010010;
        4'b0110: seg = 7'b0000010;
        4'b0111: seg = 7'b111000;
        4'b1000: seg = 7'b0000000;
        4'b1001: seg = 7'b0011000;
        4'b1010: seg = 7'b0001000;
        4'b1011: seg = 7'b0000011;
        4'b1101: seg = 7'b0100001;
        4'b1110: seg = 7'b0000110;
        4'b1111: seg = 7'b0001110;
```

Figure 1.3: *always\_comb* block describing the behavior of the circuit

### 3) Design and Sim Code

```
module SevenSegDisplayDesign(  
    input [3:0] binary,  
    output logic [6:0] seg  
);  
  
    always_comb  
    begin  
        case(binary)  
            4'b0000: seg = 7'b1000000;  
            4'b0001: seg = 7'b1111001;  
            4'b0010: seg = 7'b0100100;  
            4'b0011: seg = 7'b0110000;  
            4'b0100: seg = 7'b0011001;  
            4'b0101: seg = 7'b0010010;  
            4'b0110: seg = 7'b0000010;  
            4'b0111: seg = 7'b1111000;  
            4'b1000: seg = 7'b0000000;  
            4'b1001: seg = 7'b0011000;  
            4'b1010: seg = 7'b0001000;  
            4'b1011: seg = 7'b0000011;  
            4'b1101: seg = 7'b0100001;  
            4'b1110: seg = 7'b0000110;  
            4'b1111: seg = 7'b0001110;  
        endcase  
    end  
endmodule
```

```

module SevenSegDisplaySim();
    logic [3:0] binary;
    logic [6:0] seg;

    SevenSegDisplayDesign SevenSegDisplayDesign_inst(.*);
    initial
    begin
        for (int i = 0; i < 16; i++)
        begin
            binary = i;
            #10;
        end
    end
endmodule

```

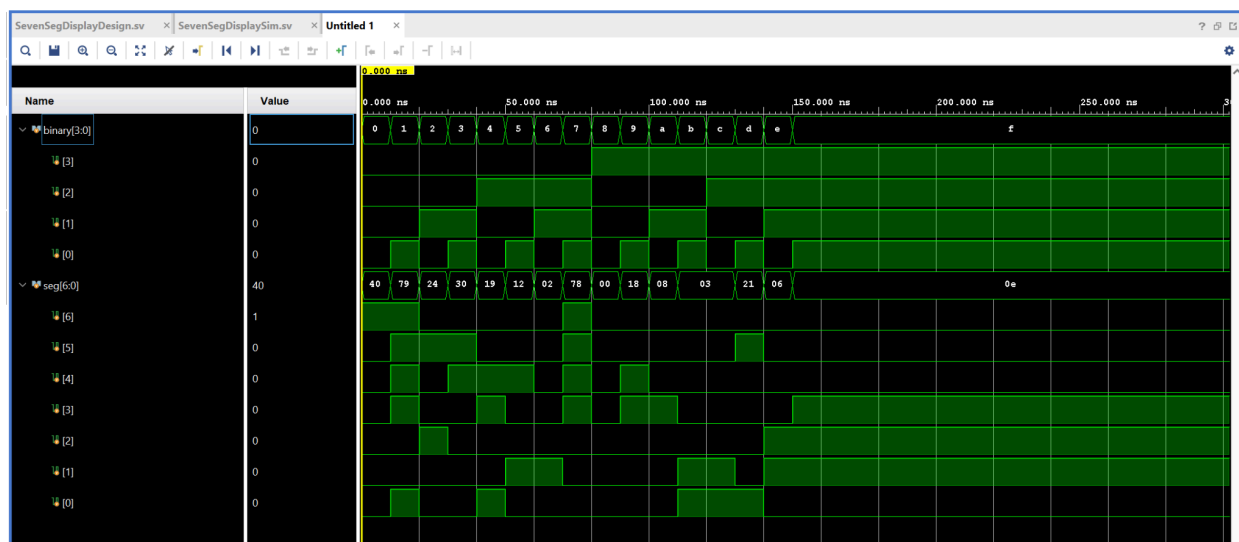


Figure 1.4: Design Code, Sim Code, and Timing Diagram

## Part 2: 2x1 MUX

### 1) MUX Behavior Model

```
module 2X1MUXDesign # (parameter width = 4) (  
    Input [WIDTH -1:0] zero,  
    Input [WIDTH -1:0] one,  
    Input sel,  
    Output logic [WIDTH -1:0] mux_out);  
    always_comb  
    begin  
        if (sel == 1)  
            mux_out = one;  
        else  
            mux_out = zero;  
        end  
    end  
end
```

### 2) Code and Timing Diagram

#### - Design Code

```
module MUXDesign #(parameter WIDTH=4)(  
    input [WIDTH -1:0] one,  
    input [WIDTH -1:0] zero,  
    input sel,  
    output logic [WIDTH -1:0] mux_out  
);  
  
    always_comb  
    begin  
        if (sel == 1)  
            mux_out = one;  
        else  
            mux_out = zero;  
        end  
    end  
endmodule
```

#### - Sim Code

```

module MUXSim();
    logic [3:0] zero = 4'b1110;
    logic [3:0] one = 4'b1111;
    logic [3:0] mux_out
    logic sel;
    MUXDesign #(4) MUXSim(. *);
    initial begin
        $display ("Begin MUXSim");
        sel = 0;
        #10;

        sel = 1;
        #10;

        end

endmodule

```

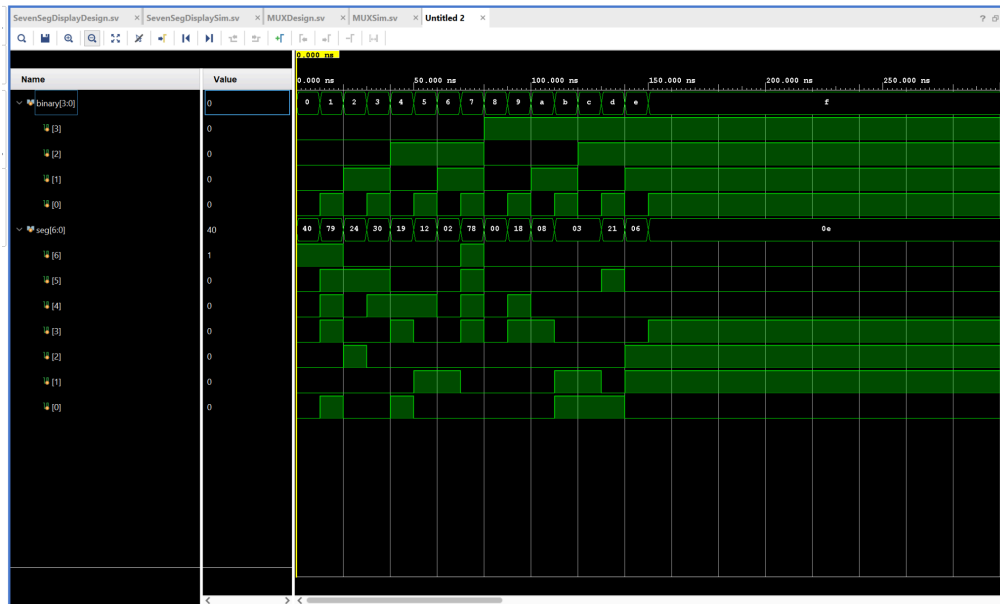


Figure 2.1: Timing Diagram for MUX

### Part 3: Top Level Module

 


Figure 3.1: BBD For the Top Level Module. Not pictured: A = 4 bits, B = 4 Bits, Seg = 7 bits, An = 4 bits.

- 1) Code for Top Level Design, Sim, and Constraints (modified section)



```

module TopLevelDesign (
    input [3:0] A,
    input [3:0] B,
    output [6:0] seg,
    output [3:0] an
);

    logic [3:0] S;
    logic Co;

    RCASource RCASource_inst (.*);

    SevenSegDisplayDesign SS1 (.binary(S),.seg(seg));

    MUXDesign #(4)MUXDesign(.zero(4'b1110),.one(4'b1111),.sel(Co),.mux_out(an));
endmodule

```

```

module TopLevelSim();

```

```

logic [3:0] A, B;
logic [3:0] an;
logic [6:0] seg;
logic C;

RCASource RCASource_inst(.*);
SevenSegDeisplaySim SS1 (.binary(S),.seg(seg));
mux2#(4)MUXDesign(.zero(4'b1110),.one(4'b1111),.sel(C),.mux_out(an));

initial
begin

//test 1
A = 5;
B = 3;
#10
if ( S !== 8 && C0 !== 0 && an !== 0) $display ("Error A%h B%h", A, B);

//test 2
A = 8;
B = 9;
#10
if ( S !== 1 && C0 !== 1) $display ("Error A%h B%h", A, B);

$display("Finished");
end

endmodule

```

#7 segment display

```
set_property PACKAGE_PIN W7 [get_ports {seg[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {seg[0]}]
set_property PACKAGE_PIN W6 [get_ports {seg[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {seg[1]}]
set_property PACKAGE_PIN U8 [get_ports {seg[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {seg[2]}]
set_property PACKAGE_PIN V8 [get_ports {seg[3]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {seg[3]}]
set_property PACKAGE_PIN U5 [get_ports {seg[4]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {seg[4]}]
set_property PACKAGE_PIN V5 [get_ports {seg[5]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {seg[5]}]
set_property PACKAGE_PIN U7 [get_ports {seg[6]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {seg[6]}]
```

```
#set_property PACKAGE_PIN V7 [get_ports dp]
    #set_property IOSTANDARD LVCMOS33 [get_ports dp]
```

```
set_property PACKAGE_PIN U2 [get_ports {an[0]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {an[0]}]
set_property PACKAGE_PIN U4 [get_ports {an[1]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {an[1]}]
set_property PACKAGE_PIN V4 [get_ports {an[2]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {an[2]}]
set_property PACKAGE_PIN W4 [get_ports {an[3]}]
    set_property IOSTANDARD LVCMOS33 [get_ports {an[3]}]
```

