

Part 1

Description:

- In this lab, we will create a simple calculator that will be able to add and subtract 4 bit signed binary numbers, and display the output as a hex digit on the seven-segment display only if the output is valid, and otherwise turn the display off.

 


Figure 1.1.0: Top Level black box diagram

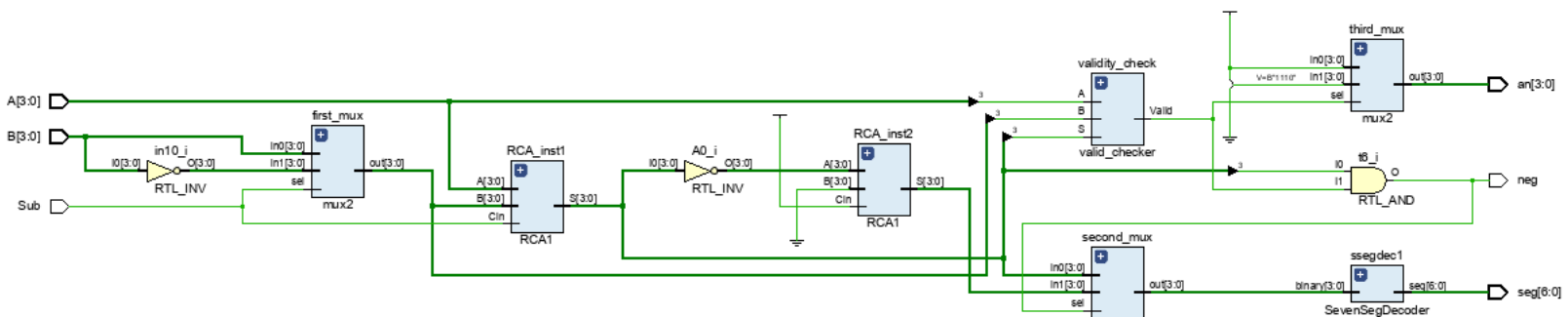


Figure 1.1.1: Top Level Structural Model/Schematic

 


Figure 1.1.2: Top Level timing diagram of test cases

Figure 1.1.3: Timing diagram for the seven segment decoder. Showcases all possible inputs and their outputs.

Design Code for Top Level:

```

module Lab4 (
    input [3:0] A ,
    input [3:0] B ,
    input Sub,
    output [6:0] seg,
    output [3:0] an,
    output neg );

    logic [3:0] t1;
    logic [3:0] t3;
    logic [3:0] t4;
    logic [3:0] t5;
    logic t6;
    logic t7;

```

```
assign t6 = t3[3] & t7;  
assign neg = t6;
```

```
RCA1 RCA_inst1 (.A(A), .B(t1),.Cin(Sub), .S(t3), .C0());  
mux2 first_mux(.in0(B),.in1(~B),.sel(Sub),.out(t1));  
RCA1 RCA_inst2 (.A(~t3),.B(4'b0000),.Cin(1),.S(t4), .C0());  
mux2 second_mux(.in0(t3),.in1(t4),.sel(t6),.out(t5));  
valid_checker validity_check(.A(A[3]),.B(t1[3]),.S(t3[3]),.Valid(t7));  
mux2 third_mux(.in0(4'b1111),.in1(4'b1110),.sel(t7),.out(an));  
SevenSegDecoder ssegdec1(.binary(t5),.seg(seg));
```

```
endmodule
```

Simulation Code for Top Level:

```
module Lab4sim();  
    logic [3:0]A,B;  
    logic Sub;  
    logic [6:0]seg;  
    logic [3:0] an;  
    logic neg;  
    Lab4 Lab4_inst(.A(A), .B(B), .Sub(Sub), .seg(seg), .an(an), .neg(neg) );  
    initial  
    begin  
  
        A = 2; B = 1; Sub = 1;  
        #10  
        //if(Sub!=1)$display("Error", A, B, Sub);  
        A = 2; B = 1; Sub = 0;  
        #10  
        // if(Sub!=0)$display("Error", A, B, Sub);  
        A = 7; B = 4; Sub = 1;  
        #10  
        //if(Sub!=0)$display("Error", A, B, Sub);  
        A = 7; B = -8; Sub = 1;  
        #10  
        A = -8; B = -7; Sub = 0;  
        #10  
        // if(Sub!=0)$display("Error", A, B, Sub);  
        A = -8; B = -8; Sub = 1;  
        #10  
        //if(Sub!=1)$display("Error", A, B, Sub);
```

```
A = -8; B = -8; Sub = 0;
#10
//if(Sub!=0)$display("Error", A, B, Sub);
A = -4; B = -4; Sub = 1;
#10
//if(Sub!=1)$display("Error", A, B, Sub);
A = -4; B = -4; Sub = 0;
#10
//if(Sub!= 0)$display("Error", A, B, Sub);

$display("Finished");
end
```

Part 2

This part covers the design of the validity checker module that outputs a '1' when the result is valid.

 


Figure 1.2.0: Black Box Diagram showing the validity checker's 3 inputs and single output.

index	A[3]	t1[3]	t3[3]	Valid
0	0	0	0	1
1	0	0	1	0
2	0	1	0	1
3	0	1	1	1
4	1	0	0	1
5	1	0	1	1
6	1	1	0	0
7	1	1	1	1

Figure 1.2.1: Truth table representing the boolean logic present in the validity checker.

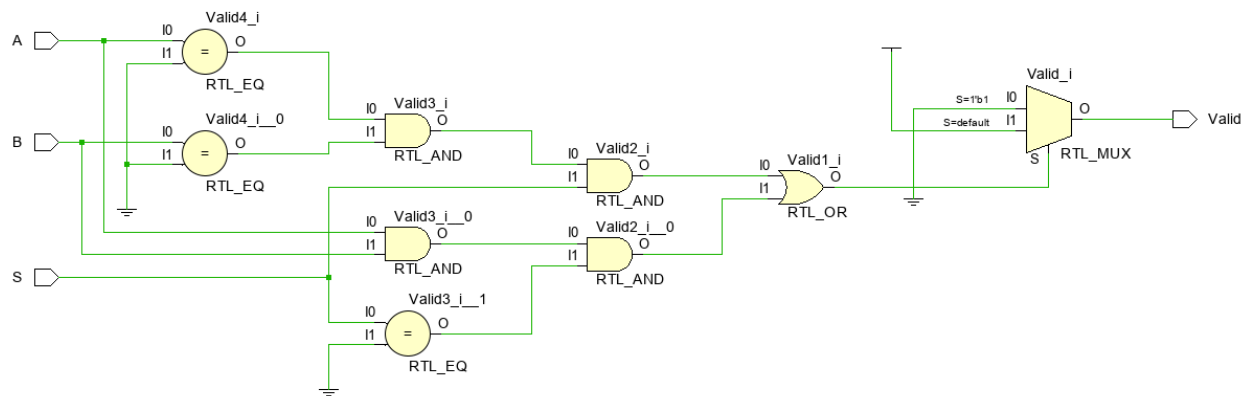


Figure 1.2.2: Circuit schematic of the validity checker

 


Figure 1.2.2: Timing diagram for the validity checker. Showcases all possible inputs and their outputs.

Validity Checker Design Code:

```

module valid_checker(
    input A,
    input B,
    input S,
    output logic Valid );
    always_comb
    begin
        begin
            if((A == 0 && B == 0 && S == 1) || (A==1 && B==1 && S == 0))
                Valid = 0;
            else
                Valid = 1;
        end
    end
end

```

```
endmodule
```

```
Validity Checker Sim Code:
```

```
module validity_checksim();
```

```
    logic A,B,S,Valid;
```

```
    valid_checker validity_check_inst(. *);
```

```
initial
```

```
begin
```

```
    A = 0; B = 0; S = 0;
```

```
    #10
```

```
    if(Valid!=1)$display("Error", A, B, S);
```

```
    A = 0; B = 0; S = 1;
```

```
    #10
```

```
    if(Valid!=0)$display("Error", A, B, S);
```

```
    A = 0; B = 1; S = 0;
```

```
    #10
```

```
    if(Valid!=1)$display("Error", A, B, S);
```

```
    A = 0; B = 1; S = 1;
```

```
    #10
```

```
    if(Valid!=1)$display("Error", A, B, S);
```

```
    A = 1; B = 0; S = 0;
```

```
    #10
```

```
    if(Valid!=1)$display("Error", A, B, S);
```

```
    A = 1; B = 0; S = 1;
```

```
    #10
```

```
    if(Valid!=1)$display("Error", A, B, S);
```

```
    A = 1; B = 1; S = 0;
```

```
    #10
```

```
    if(Valid!=0)$display("Error", A, B, S);
```

```
    A = 1; B = 1; S = 1;
```

```
    #10
```

```
    if(Valid!=1)$display("Error", A, B, S);
```

```
    $display("Finished");
```

```
end
```

```
endmodule
```

Part 3

In this part of the lab, the RCA is updated with a new input, Cin.

 


Figure 1.3.0: Black Box Diagram for the updated RCA showing the new input, Cin.

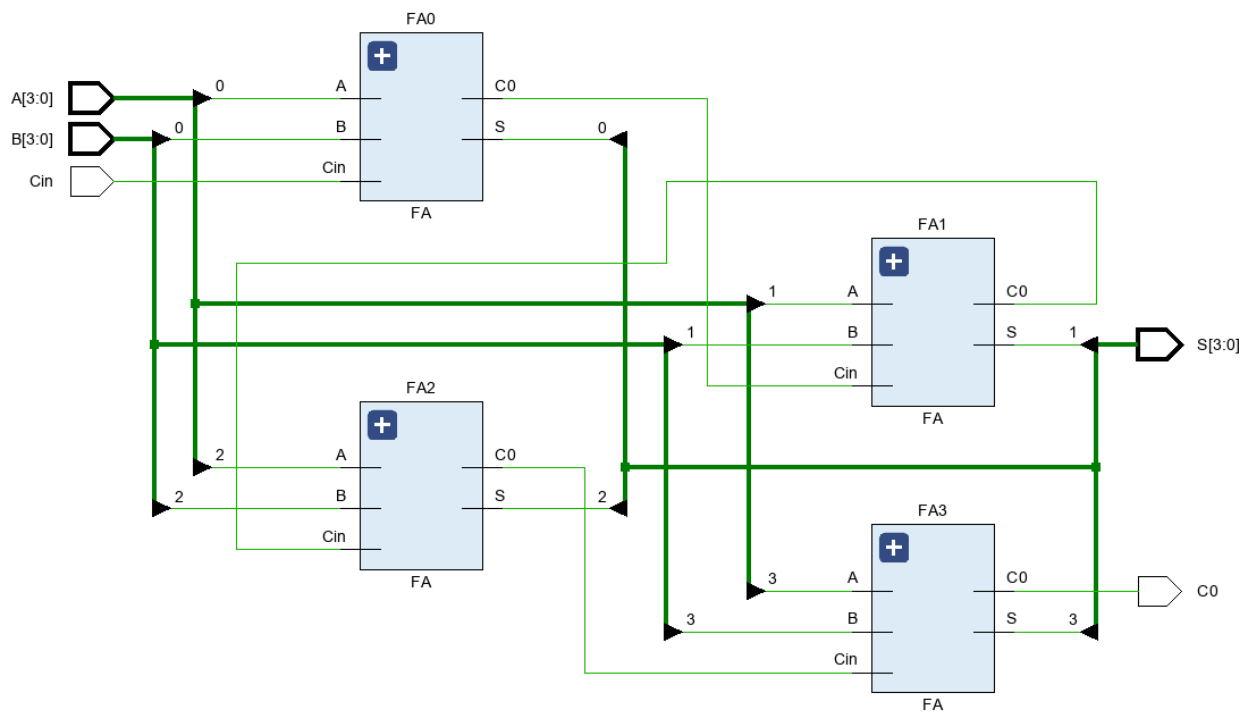


Figure 1.3.1: Schematic diagram of the RCA circuit.

 


Figure 1.3.2: Timing diagram for the new, updated RCA.

RCA Design Code:

```

module RCA1(
    input [3:0] A,
    input [3:0] B,
    input Cin,
    output [3:0] S,
    output C0
);
    logic t1,t2,t3;

    FA FA0 (.A(A[0]), .B(B[0]), .Cin(Cin), .S(S[0]), .C0(t1));
    FA FA1 (.A(A[1]), .B(B[1]), .Cin(t1), .S(S[1]), .C0(t2));
    FA FA2 (.A(A[2]), .B(B[2]), .Cin(t2), .S(S[2]), .C0(t3));
    FA FA3 (.A(A[3]), .B(B[3]), .Cin(t3), .S(S[3]), .C0(C0));

endmodule

```